 


Computer Architecture & Microprocessor System

COMBINATIONAL LOGIC DESIGN


Dennis A. N. Gookyi






CONTENTS


❖ Combinational Logic Design

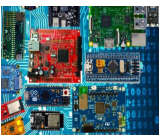

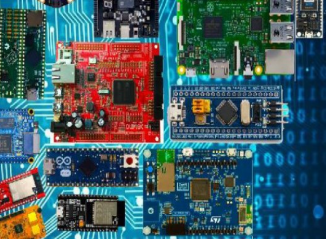

BIG PICTURE: BUILDING A PROCESSOR

❖ Single cycle processor

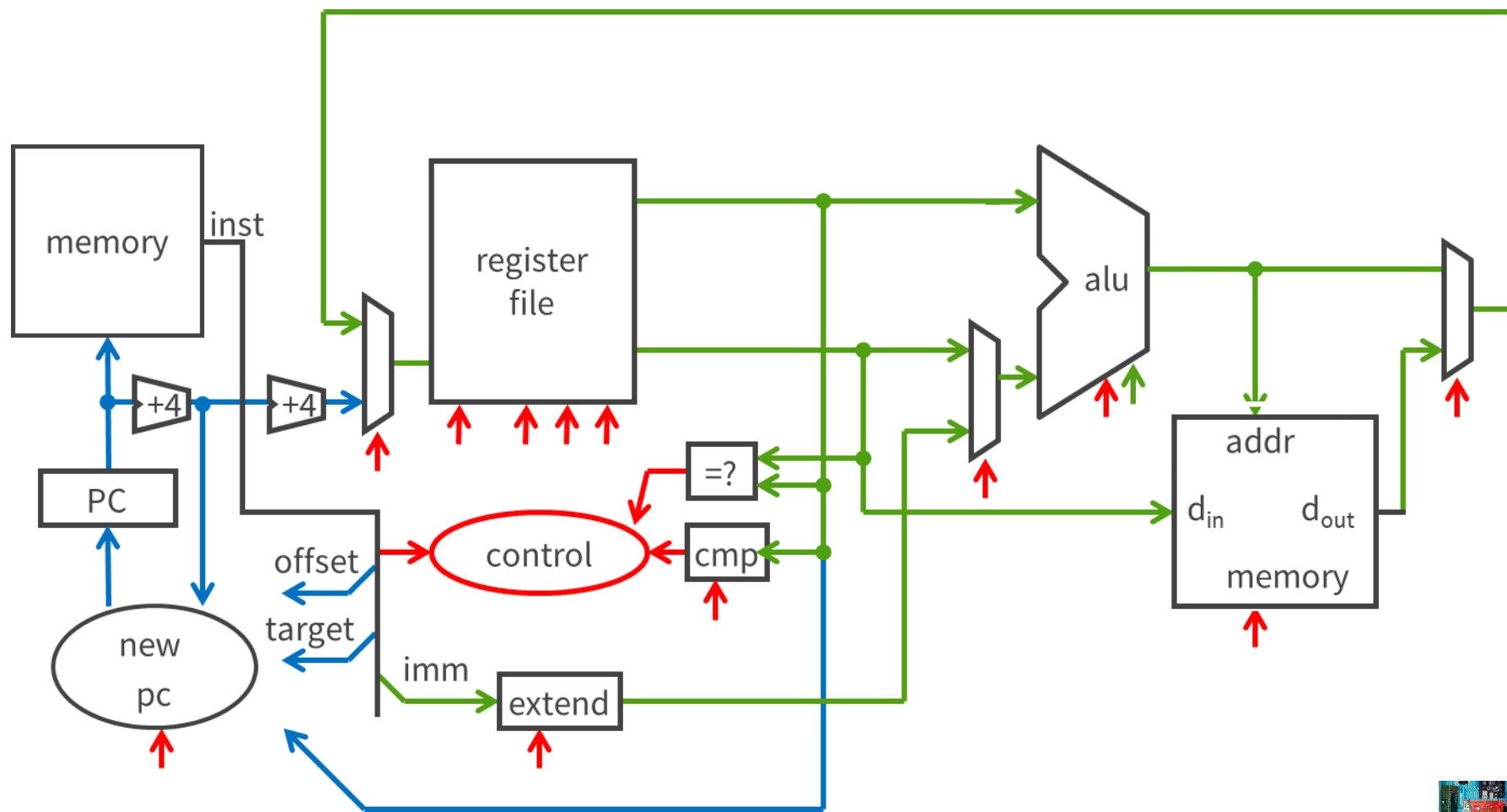

COMMON LOGIC GATES

❖ Basic Logic gates

Buffer



A	Z
0	0
1	1

AND



A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

OR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

XOR



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

Inverter



A	Z
0	1
1	0

NAND



A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

NOR




A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

XNOR




A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

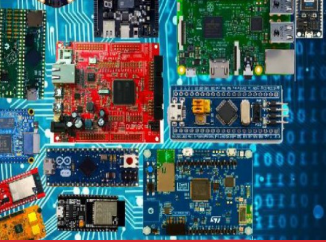

COMBINATIONAL BUILDING BLOCKS

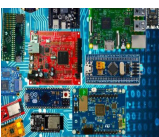- ❖ Combinational logic is often grouped into larger building blocks to build more complex systems
- ❖ Hides the unnecessary gate-level details to emphasize the function of the building block
- ❖ We now examine:
 - ☐ Decoder
 - ☐ Multiplexer
 - ☐ Full adder
 - ☐ PLA (Programmable Logic Array)






DECODER

- ❖ “Input pattern detector”
- ❖ n inputs and 2^n outputs
- ❖ Exactly one of the outputs is 1 and all the rest are 0s
- ❖ The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect
- ❖ Example: 2-to-4 decoder



A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 



DECODER

  
- ❖ n inputs and 2^n outputs
- ❖ Exactly one of the outputs is 1 and all the rest are 0s
- ❖ The output that is logically 1 is the output corresponding to the input pattern that the logic circuit is expected to detect





DECODER

 - ❖ The decoder is useful in determining how to interpret a bit pattern
 - ❑ **It could be the address of a location in memory, that the processor intends to read from**
 - ❑ **It could be an instruction in the program and the processor needs to decide what action to take (based on *instruction opcode*)**






MULTIPLEXER

- ❖ Selects one of the N inputs to connect it to the output
 - Based on the value of a $\log_2 N$ -bit control input called select
- ❖ Example: 2-to-1 MUX



S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 



MULTIPLEXER


 
 
- ❖ Selects one of the N inputs to connect it to the output
 - Based on the value of a $\log_2 N$ -bit control input called select
- ❖ Example: 2-to-1 MUX





COMPARATOR

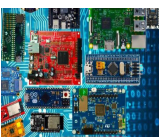  
- ❖ Equality checker (compare if equal)
- ❖ Checks if two N-input values are exactly the same
- ❖ Example: 4-bit Comparator





ARITHMETIC LOGIC UNIT (ALU)

 - ❖ Combines a variety of arithmetic and logical operations into a single unit (that performs only one function at a time)
- ❖ Usually denoted with this symbol:




ALU Symbol

ALU Operations


$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT



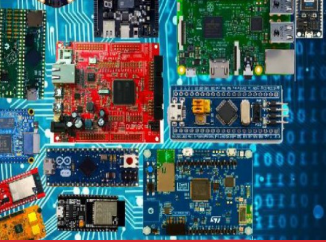


TRI-STATE BUFFER

 - ❖ A tri-state buffer enables gating of different signals onto a wire
- ❖ A tri-state buffer acts like a switch



E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

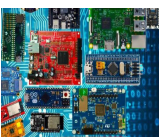
- ❖ Floating signal (Z): Signal that is not driven by any circuit
 - Open circuit, floating wire






TRI-STATE BUFFER

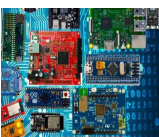- ❖ Use of tri-state buffers
- ❖ Imagine a wire connecting the CPU and memory
 - At any time only the CPU or the memory can place a value on the wire, both not both
 - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time




TRI-STATE BUFFER

❖ Use of tri-state buffers

 

TRI-STATE BUFFER


❖ Use of tri-state buffers

 



PRIORITY CIRCUIT

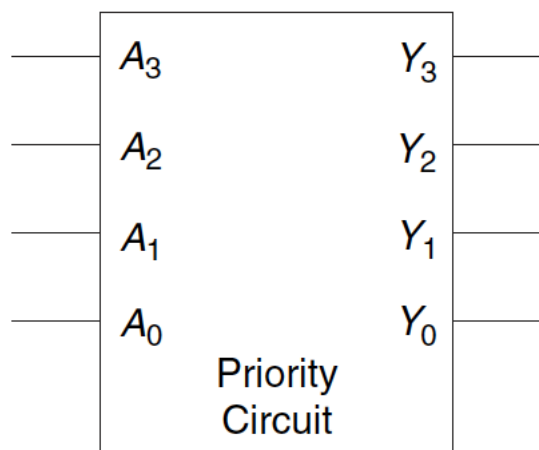- Inputs: “Requestors” with priority levels
- Outputs: “Grant” signal for each requestor
- Example 4-bit priority circuit
- Real life example: Imagine a bus requested by 4 processors



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

