 


Microprocessor System & Interfacing

MEMORY ELEMENTS


Dennis A. N. Gookyi





CONTENTS



❖ Memory Elements

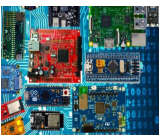




BIG PICTURE: BUILDING A PROCESSOR



❖ Single cycle processor

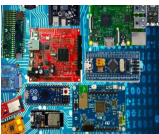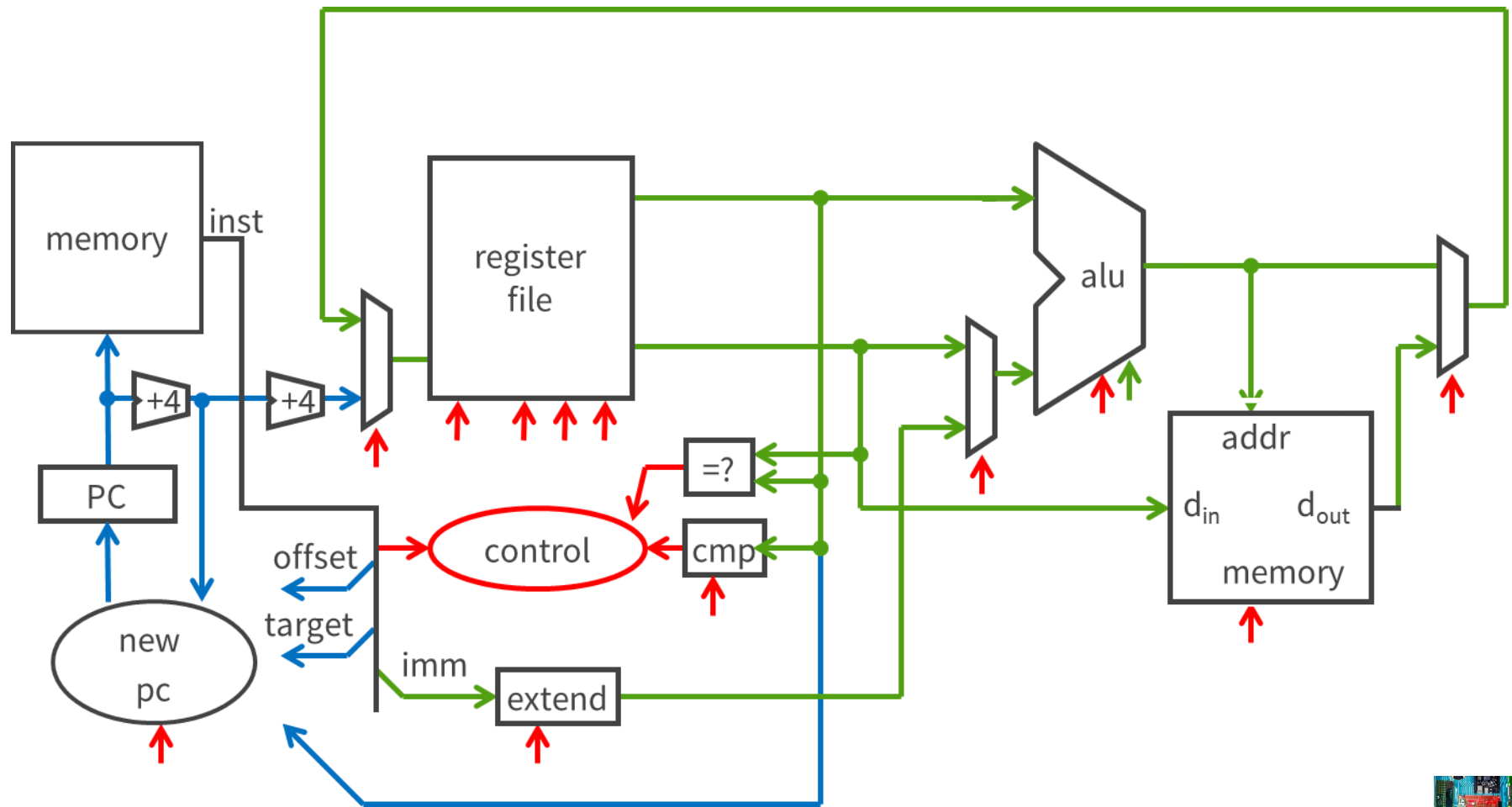

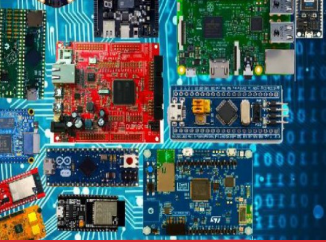

BIG PICTURE: BUILDING A PROCESSOR

❖ Single cycle processor

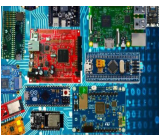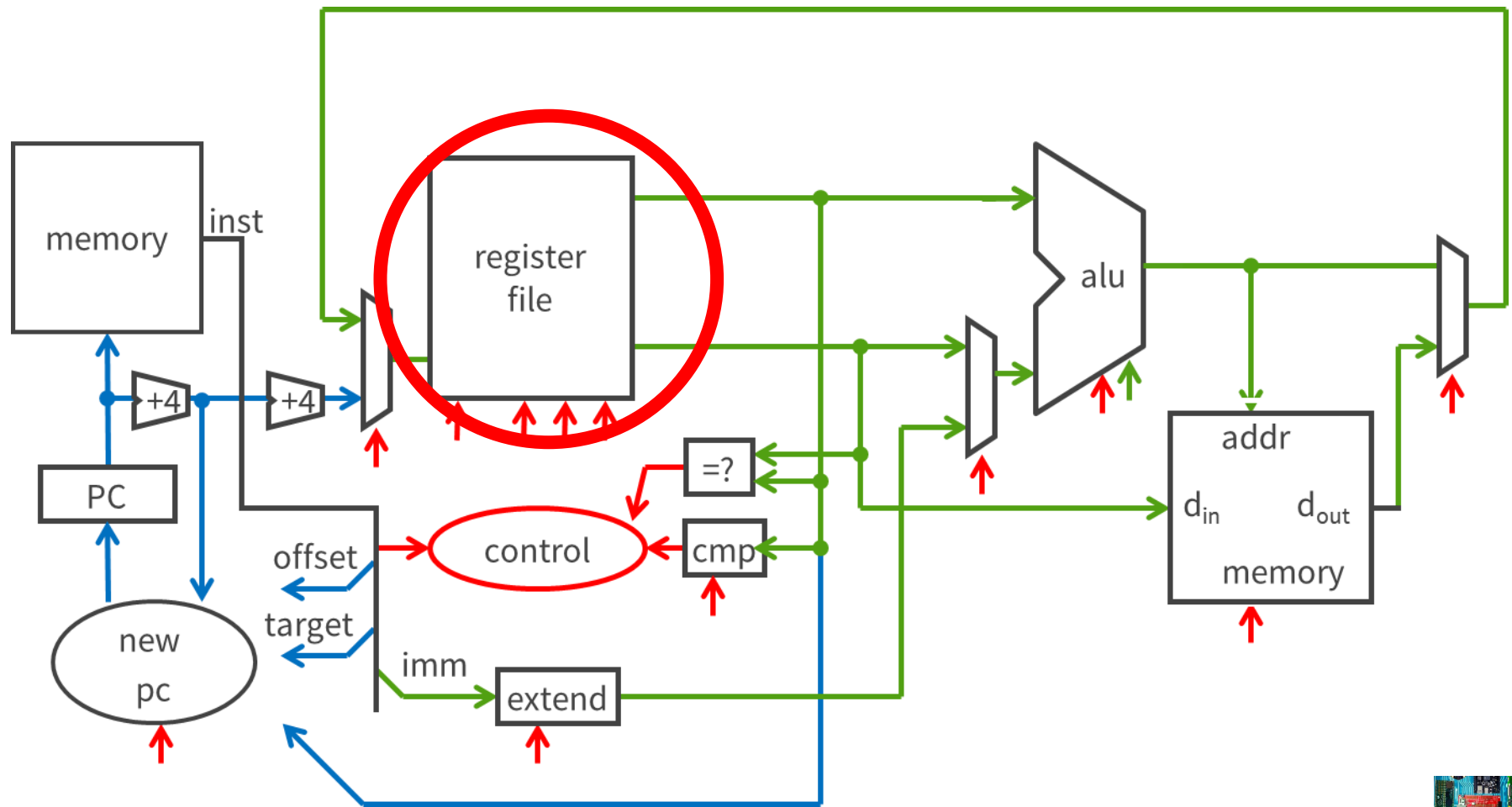




REGISTER FILE

❖ Register file

 - N read/write registers
- Indexed by register number




REGISTER FILE

❖ Register file


- N read/write registers
- Indexed by register number

`addi x1, x0, 10`

 

❖ How to write one register in the register file


- Need a decoder

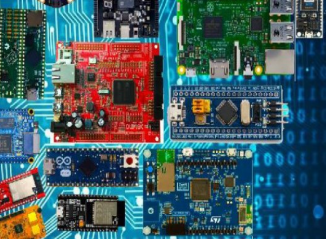


REGISTER FILE

❖ 3-to-8 decoder truth table and circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								



 


 

REGISTER FILE

❖ 3-to-8 decoder truth table and circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

   

REGISTER FILE


❖ Register file

- N read/write registers
- Indexed by register number

add x1, x0, x5

How to read from two registers?

- Need a multiplexor

 


REGISTER FILE


❖ Register file

- N read/write registers
- Indexed by register number

❖ Implementation:

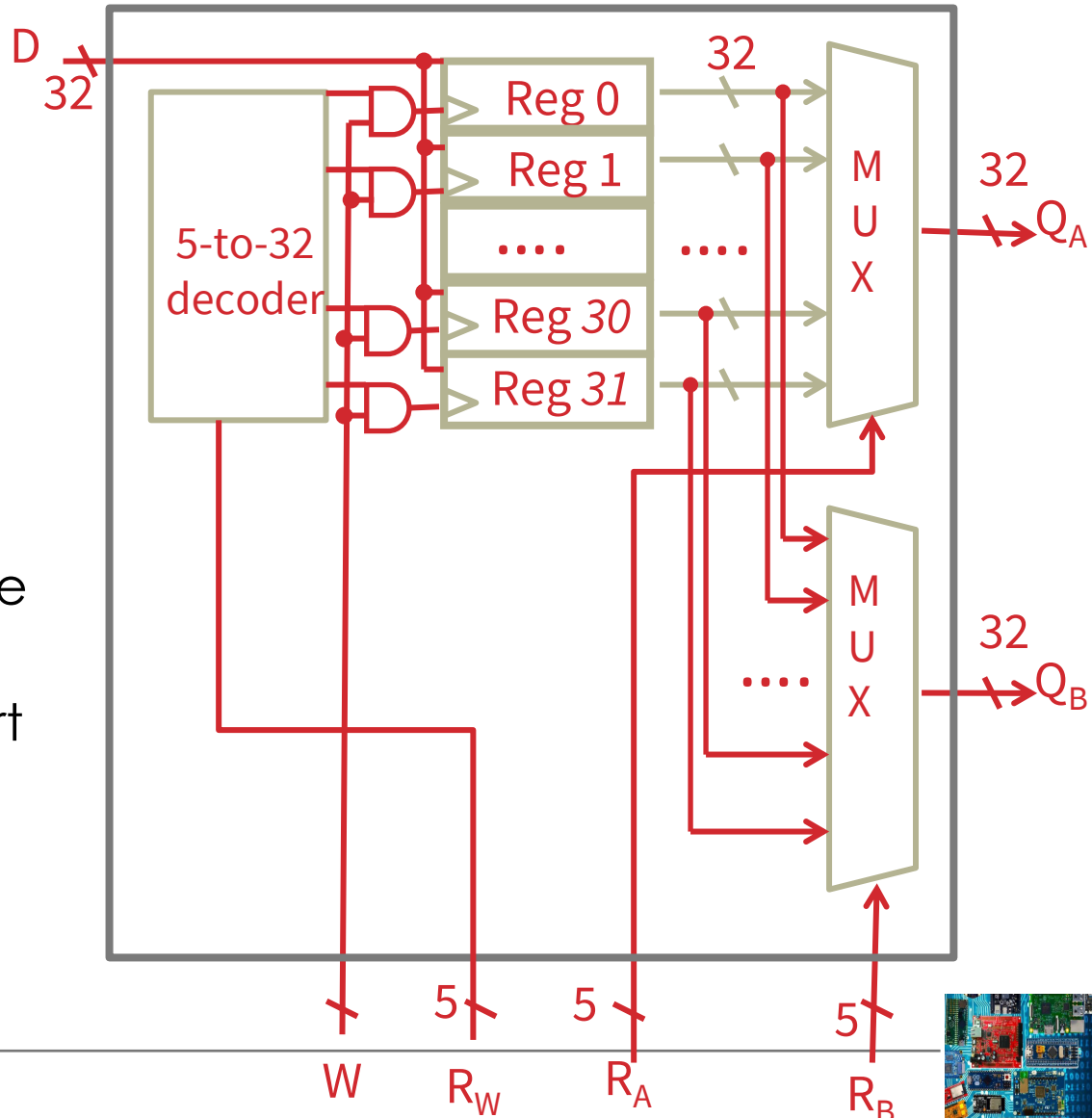- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



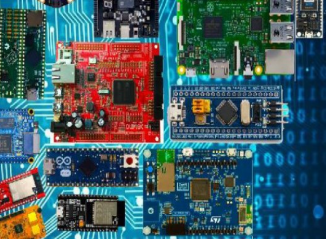


REGISTER FILE

❖ Register file

- ❑ N read/write registers
- ❑ Indexed by register number

❖ Implementation:

 - ❑ D flip flops to store bits
- ❑ Decoder for each write port
- ❑ Mux for each read port







REGISTER FILE

❖ Register file


 
- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale
e.g. 32Mb register file with 32 bit registers
Need 32x 1M-to-1 multiplexor and 32x 20-to-1M decoder
How many logic gates/transistors?




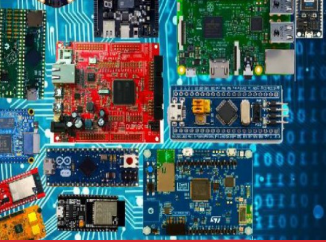

BIG PICTURE: BUILDING A PROCESSOR


❖ Single cycle processor

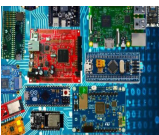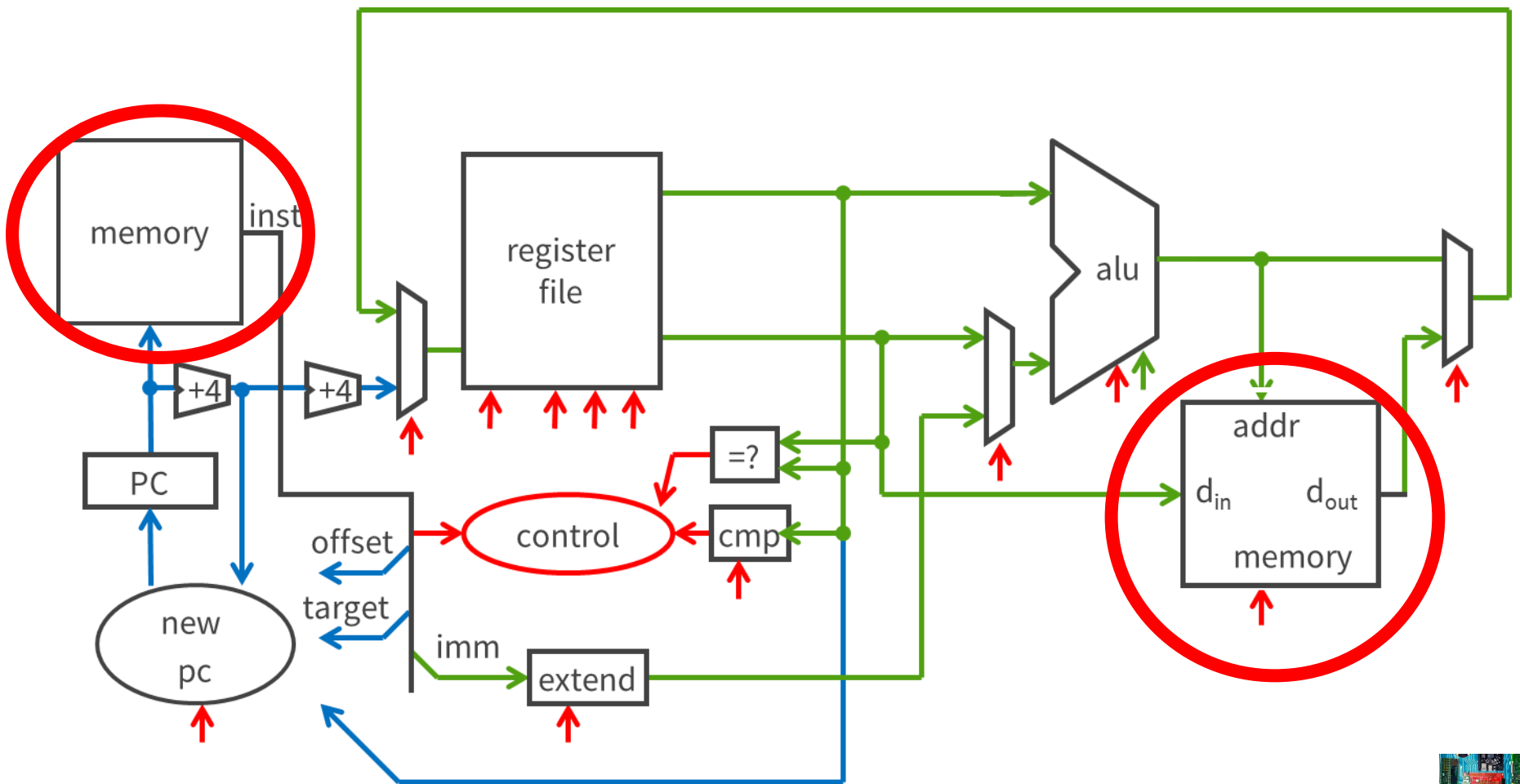

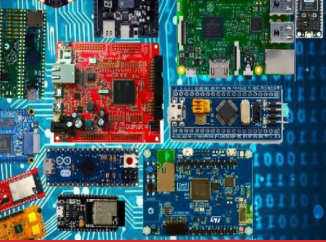


MEMORY

 - ❖ Storage Cells + bus
- ❖ Inputs: Address, Data (for writes)
- ❖ Outputs: Data (for reads)
- ❖ Also need R/W signal (not shown)



- ❖ N address bits $\rightarrow 2^N$ words total
- ❖ M data bits \rightarrow each word M bits


 
- ❖ How many address bits are necessary for a 4M x 8 SRAM module?
 - 4M word lines that are each 8 bits wide





MEMORY

 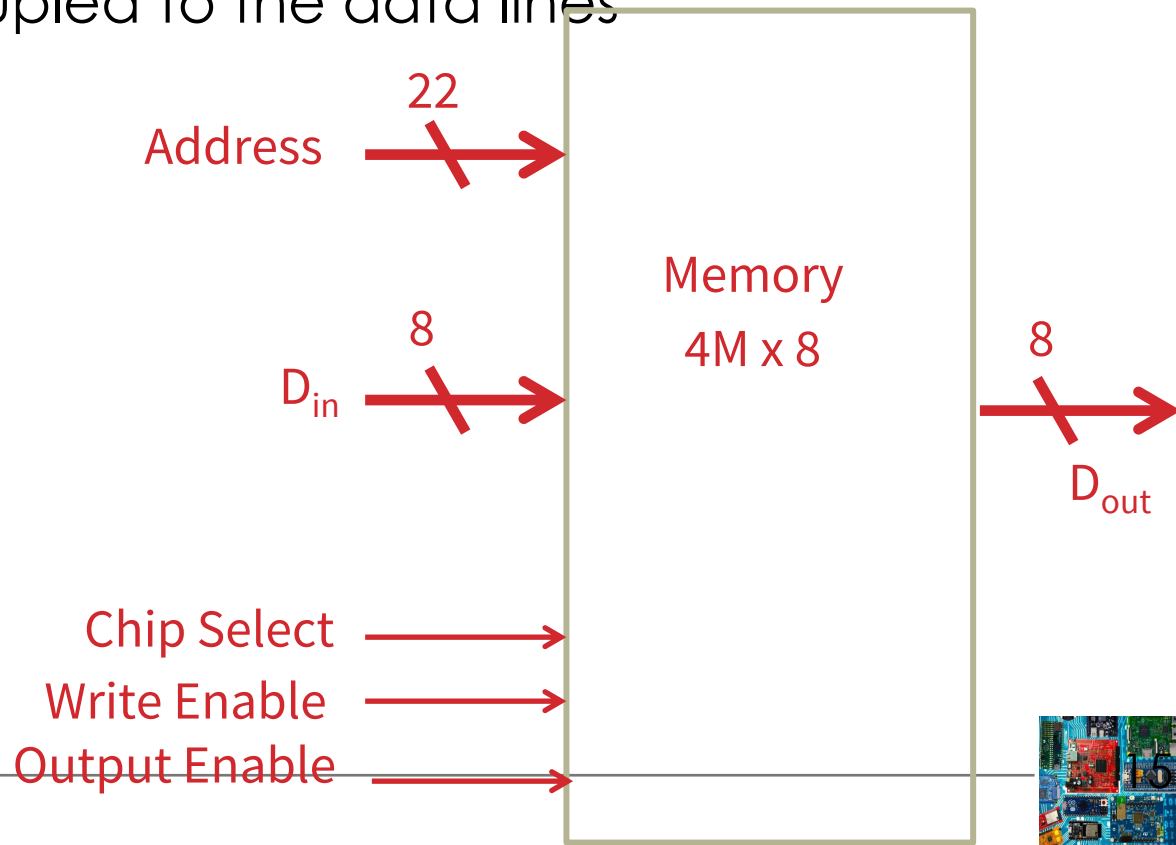
- ❖ Storage Cells + bus
- ❖ Decoder selects a word line
- ❖ R/W selector determines access type
- ❖ Word line is then coupled to the data lines



MEMORY

❖ How do we design a 4 x 2 Memory Module?



- 4 word lines that are each 2 bits wide

 

MEMORY

❖ How do we design a 4 x 2 Memory Module?



□ 4 word lines that are each 2 bits wide

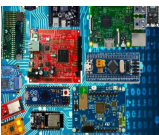 

MEMORY

❖ How do we design a 4 x 2 Memory Module?



- 4 word lines that are each 2 bits wide

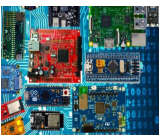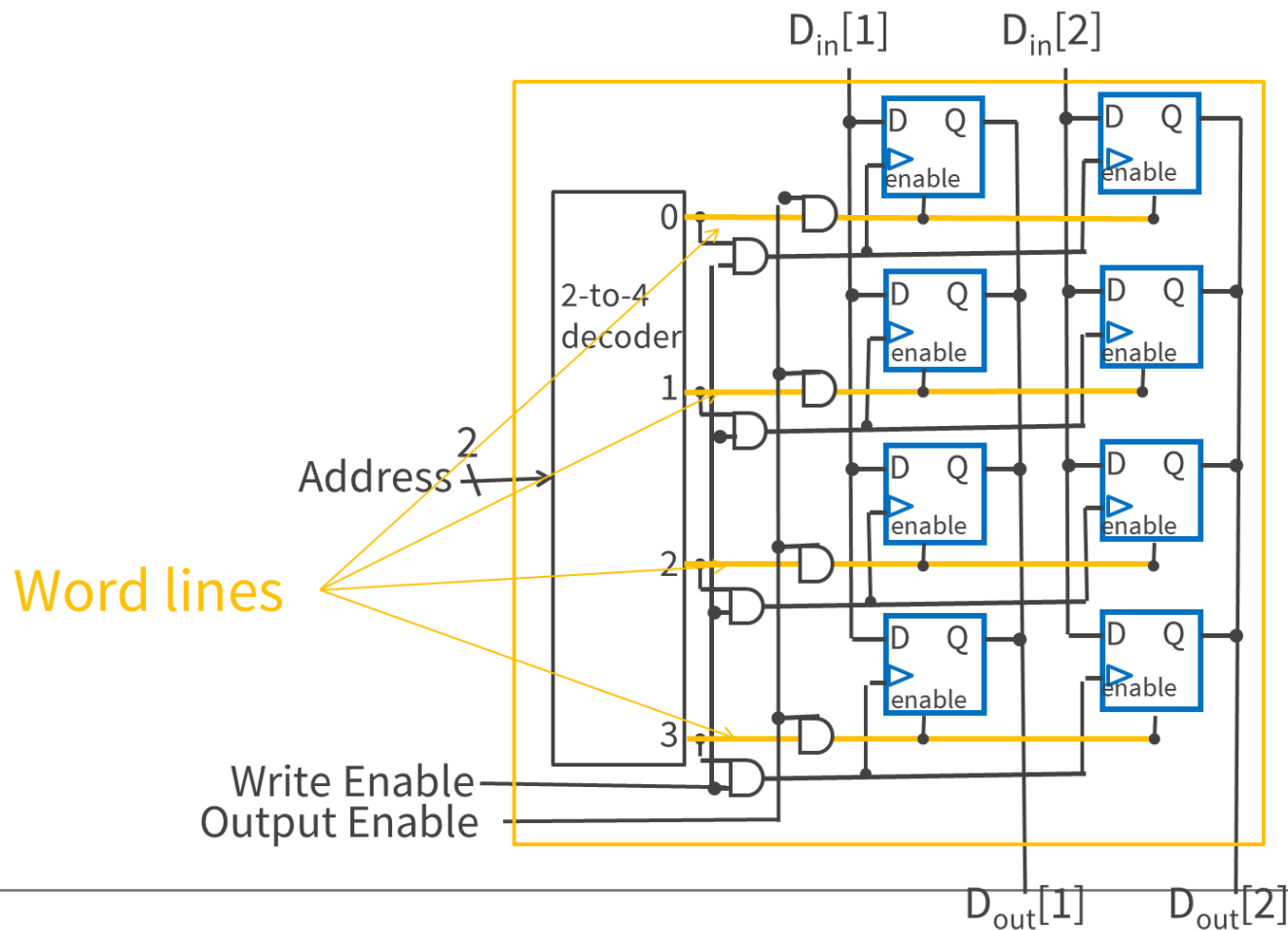

MEMORY

❖ How do we design a 4 x 2 Memory Module?


- 4 word lines that are each 2 bits wide

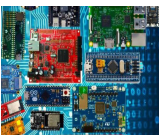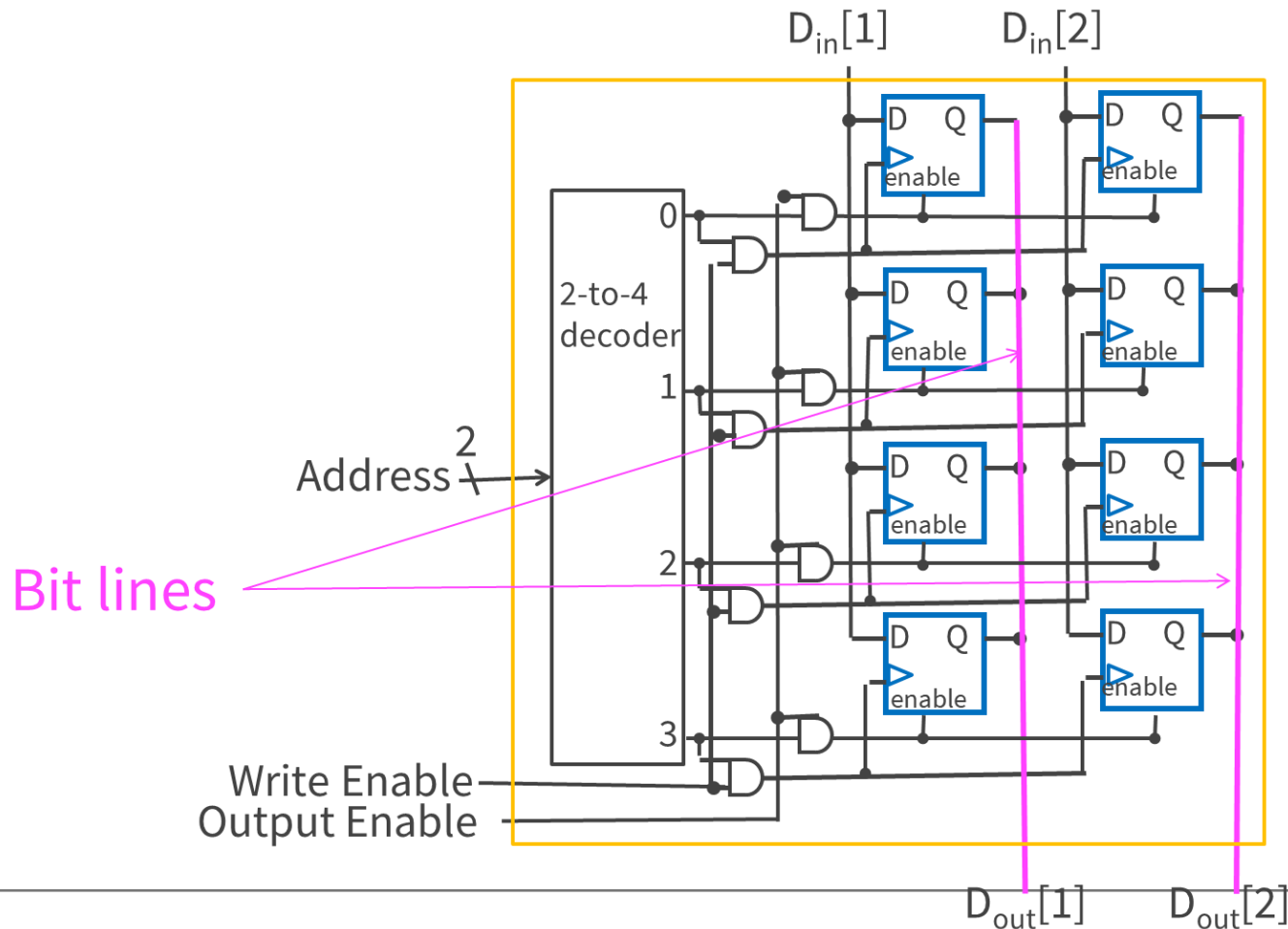

MEMORY

❖ How do we design a 4 x 2 Memory Module?


- 4 word lines that are each 2 bits wide

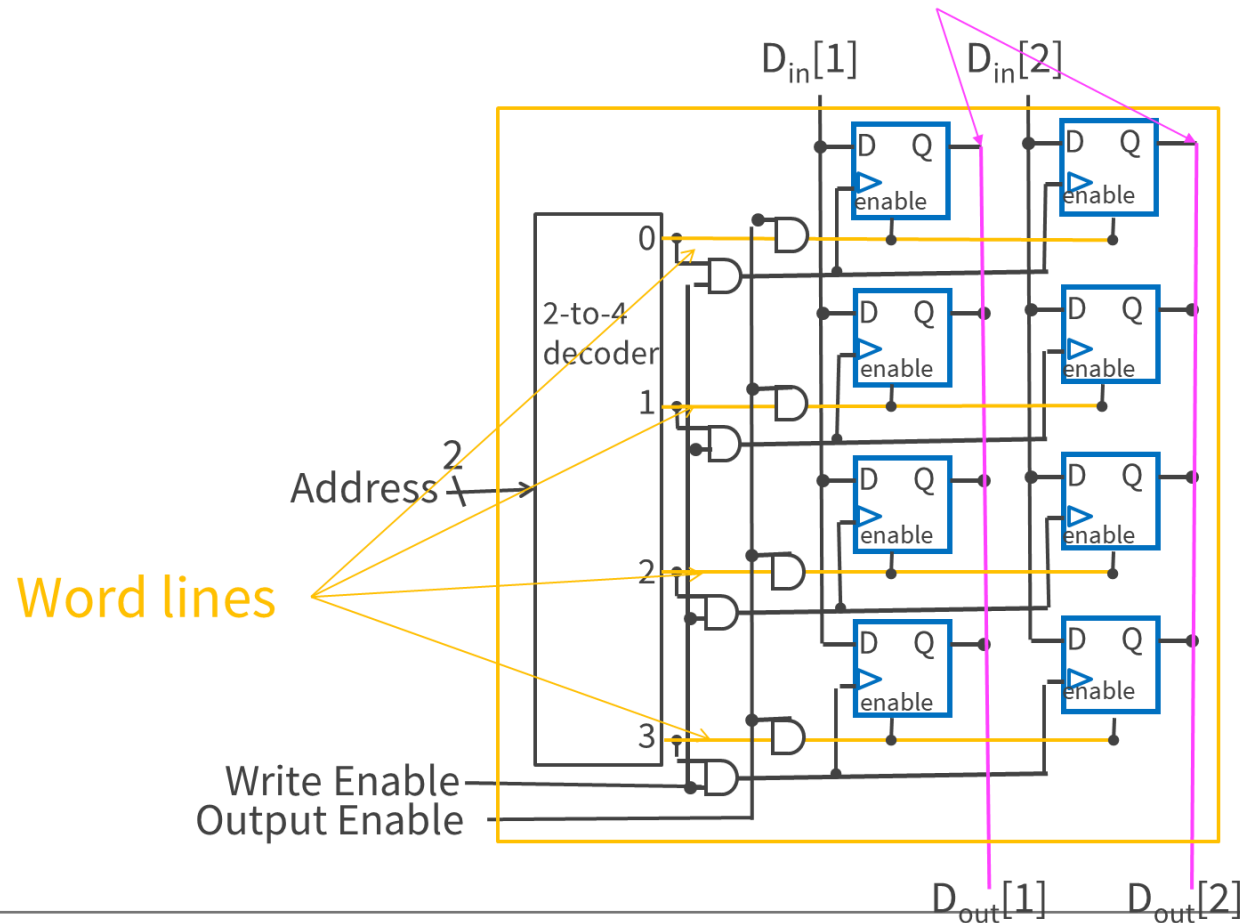

MEMORY

❖ How do we design a 4M x 8 Memory Module?

 □ 4M word lines that are each 8 bits wide $D_{in} \downarrow 8$







MEMORY

❖ How do we design a 4M x 8 Memory Module?

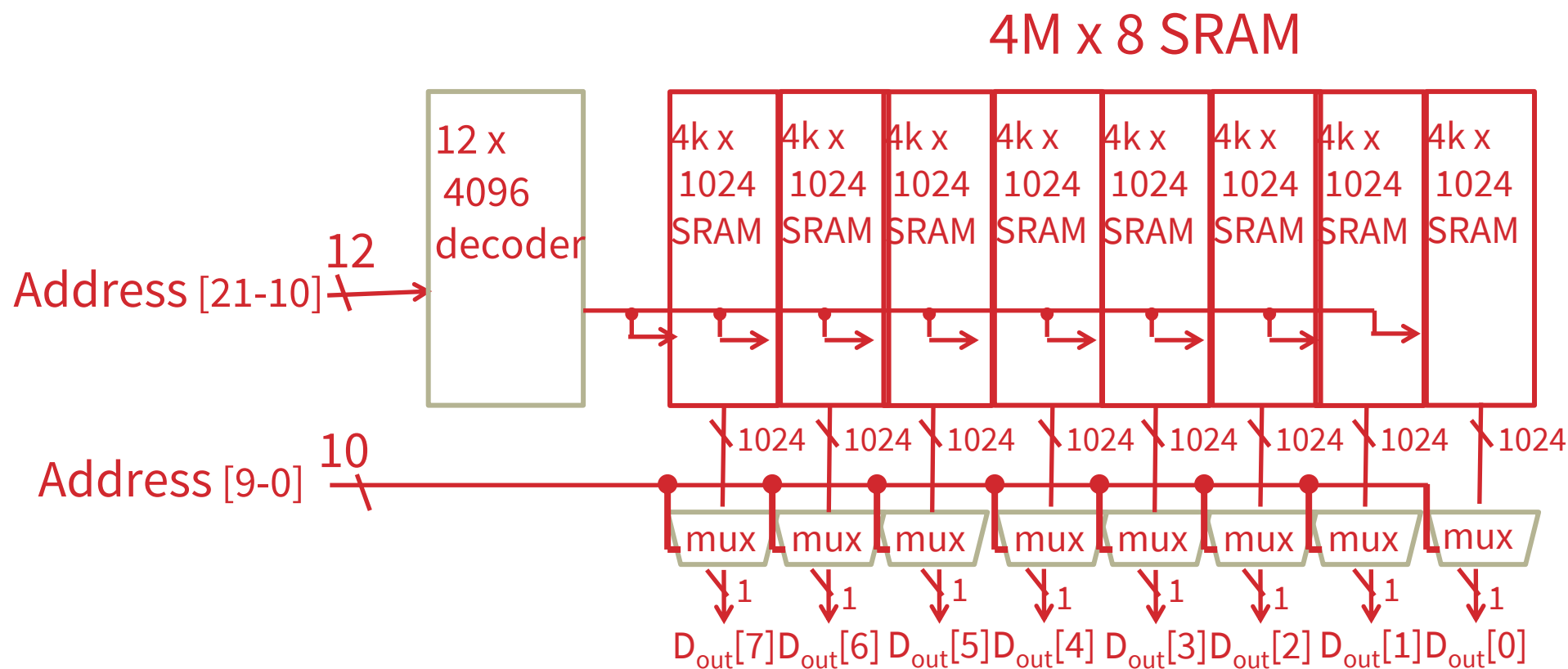- 4M word lines that are each 8 bits wide




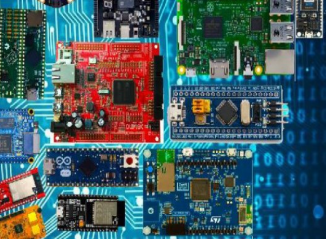


MEMORY

❖ How do we design a 4M x 8 Memory Module?

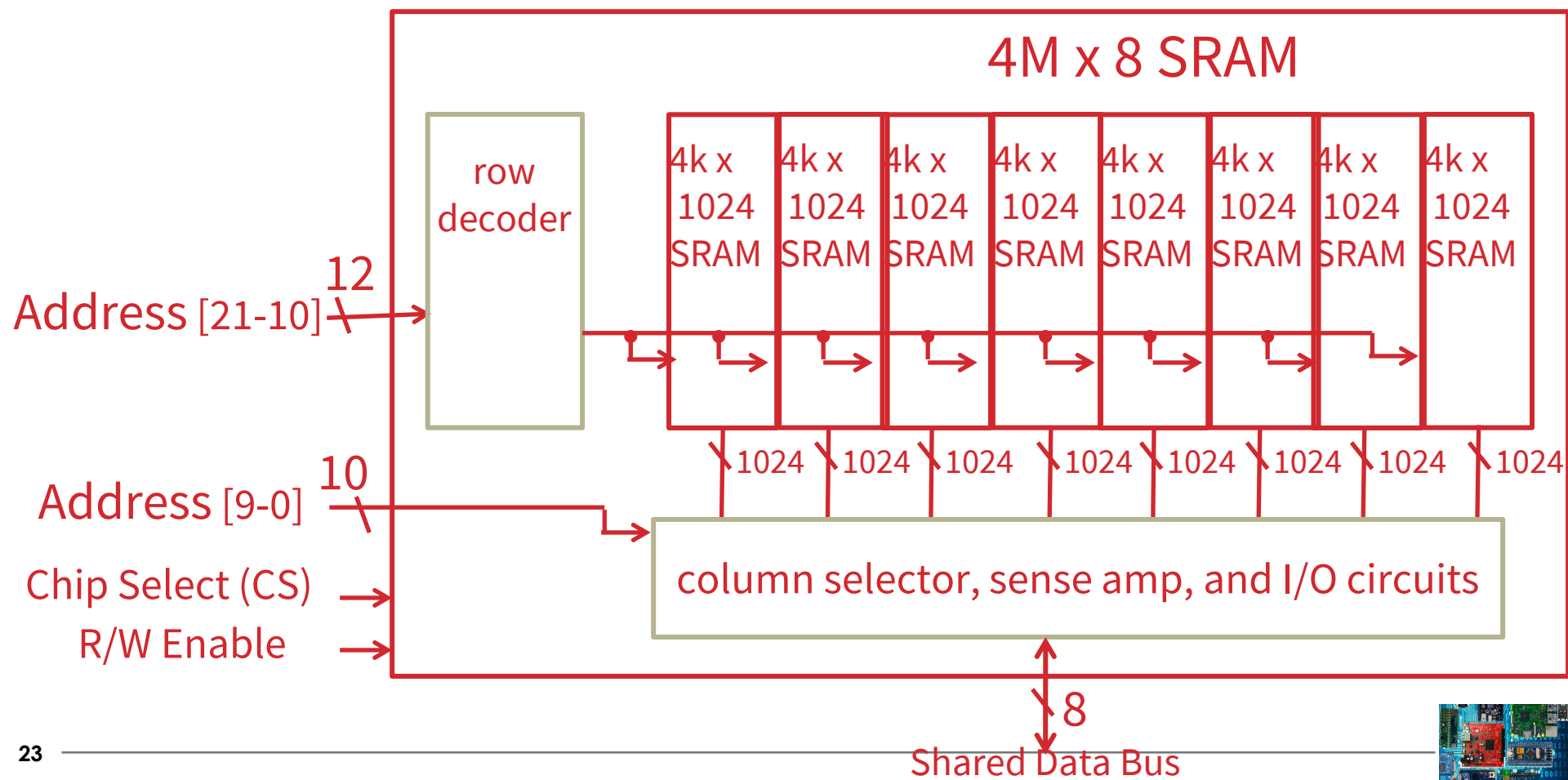- 4M word lines that are each 8 bits wide



 

MEMORY

❖ Register File tradeoffs

- ❑ + Very fast (a few gate delays for both read and write)
- ❑ + Adding extra ports is straightforward
- ❑ – Expensive, doesn't scale
- ❑ – Volatile

❖ Volatile Memory alternatives: SRAM, DRAM, ...

- ❑ – Slower
- ❑ + Cheaper, and scales well
- ❑ – Volatile

❖ Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- ❑ + Scales well
- ❑ – Limited lifetime; degrades after 100000 to 1M writes

